

# Assignment-3

## 1) Introduction

*In this lab we have extended previous lab work by displaying all 4 digit by using "clock" and "4: 1 multiplexer" for selection of any one anode activation in each cycle .*

## 2) Implementation Design

*For display of each 4 digit uniformly we have taken 20 bit vector named "refresh- timer" which is initialised to 0.*


*At each "rising edge of clock" we increment the refresh - timer value by 1 and extract "19 and 18" bits value from it.*

*These 2 bit value of refresh - timer vector can be "00" , "01" , "10" and "11" which is stored in 2 bit vector "LED - activation" and this value is used for selection from 4 different anodes basically working as 2 - bit select input for the multiplexe .*

*We have also used 4 - bit vector "which- led" to store 4 bit values from 16 - bit "Input" which is divided into 4 equal parts each consisting of 4 bits which are stored in "which - led" as per value of "LED - activation" .*


LED_activation	Anode_Activate
00	0111
01	1011
10	1101
11	1110

### *Schematic Diagram of 4digit 7 Segment LED display using clock*

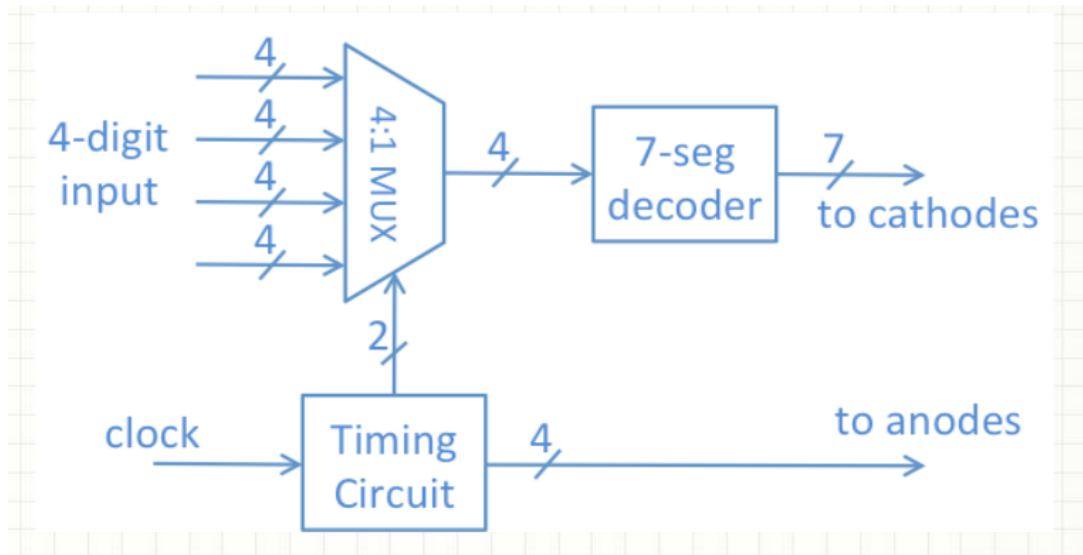

*Fig 1: Basic circuit showing use of 4: 1 MUX and clock*

## 4 Digit Seven Segment Display

 

*Fig 2 : 4 digit 7 segment display along with its anode and cathode*

### 3) Simulation Waveform for 4 digit 7 segment display

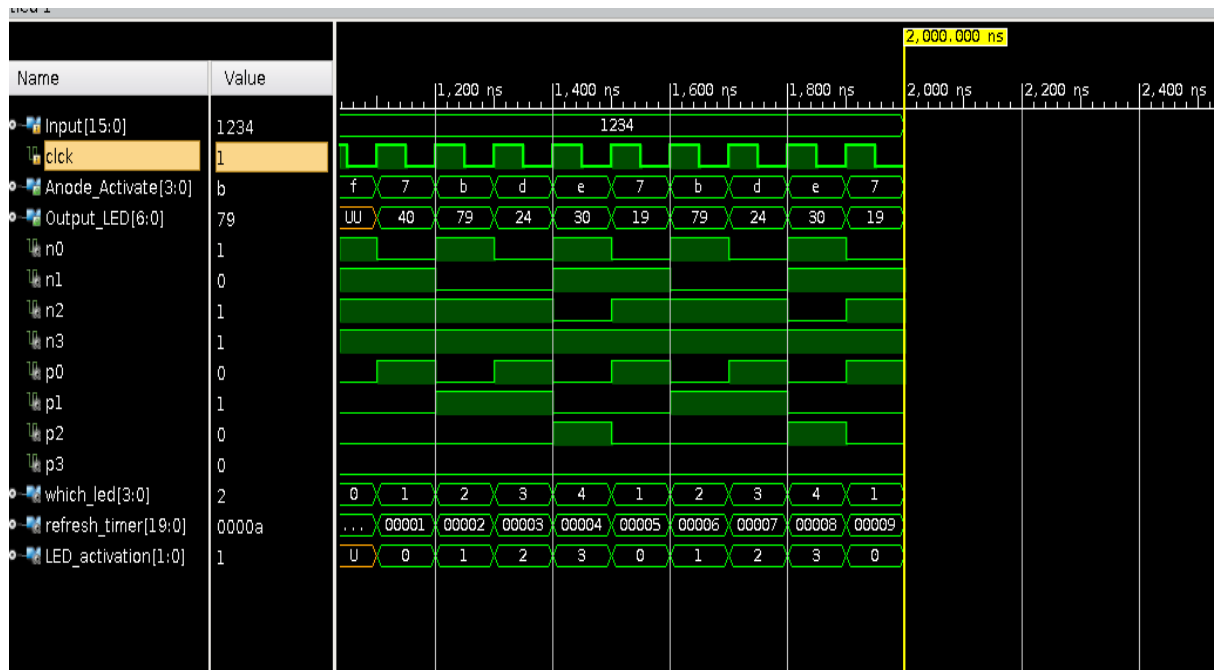


Fig 3 : Waveform of Input and Output of 4 digit – 7 segment display

#### 4) Digital Circuit for 4 – digit 7 Segment Display for displaying 4 digit


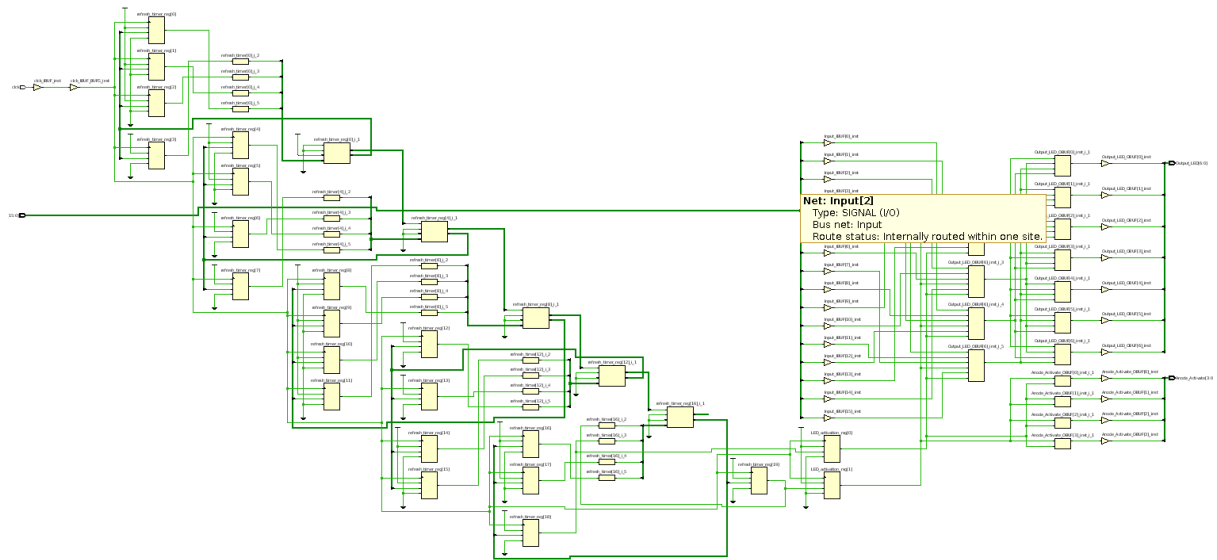


Fig 4 : Digit Circuit of 4 digit – 7 segment display each digit range from 0 – F

## 5) Resource Utilisation

- a) LUT Memory =0
- b) LUT logic = 30
- c) DSP =0
- d) Flip Flops =22
- e) BRAM = 0

## 6) Some other relevant diagram for resource utilisation

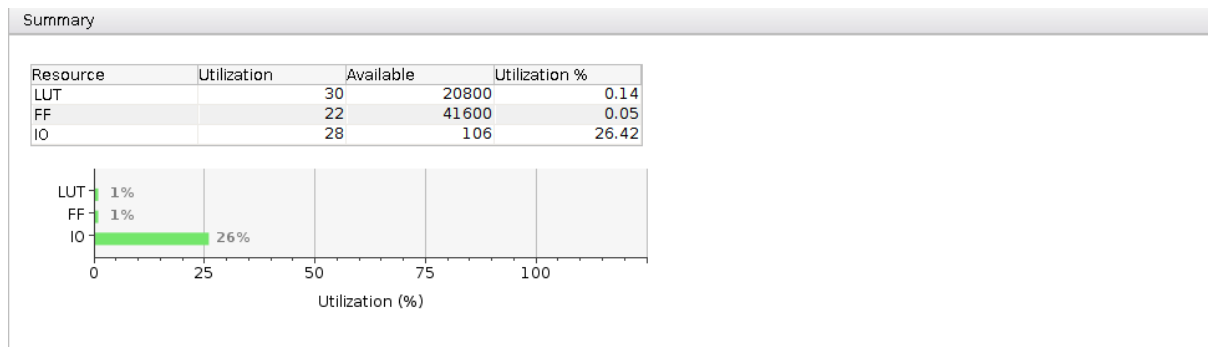

*Fig 5 : Summary*


Primitives		
Ref Name	Used	Functional Category
FDRE	22	Flop & Latch
LUT1	20	LUT
IBUF	17	IO
OBUF	11	IO
LUT4	7	LUT
CARRY4	5	CarryLogic
LUT6	4	LUT
LUT2	4	LUT
BUFG	1	Clock

*Fig 6 : Primitives*

Hierarchy				
Name	Slice LUTs (20800)	Slice Registers (41600)	Bonded IOB (106)	BUFGCTRL (32)
four_digit_display	30	22	28	1

*Fig 7 : Hierarchy*

## 7) Some photographs of FPGA Board

 

(a)