

Assignment-4

1) Introduction

In this lab we have extended previous lab work now we have to vary the LED brightness using Pulse Width Modulation (pwm) such that brightness increase as we move from right to left of the 7 segment LED display.

Pulse Width Modulation :

- a) It is technique which is used to control semiconductor devices.*
- b) It reduces average power delivered by electrical signal by converting into discrete signals.*
- c) In this technique , signal's energy is distributed through a series of pulses rather than continuous signal(as happen with analog signals).*

PWM signal generation :

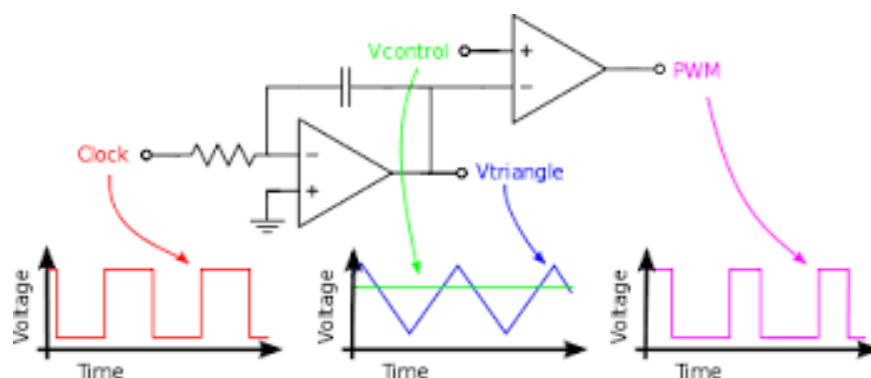


Fig 1: Circuit for generating PWM signal

Some Important Parameters related to PWM signal :

a) Duty Cycle of PWM signal :

$$\text{Duty Cycle} = \frac{\text{Turn ON time}}{\text{Turn ON time} + \text{Turn OFF time}}$$

b) Frequency of PWM signal :

$$\text{Frequency} = \frac{1}{\text{Time Period}}$$

c) Time period of PWM signal :

$$\text{Time Period} = \text{ON time} + \text{OFF time}$$

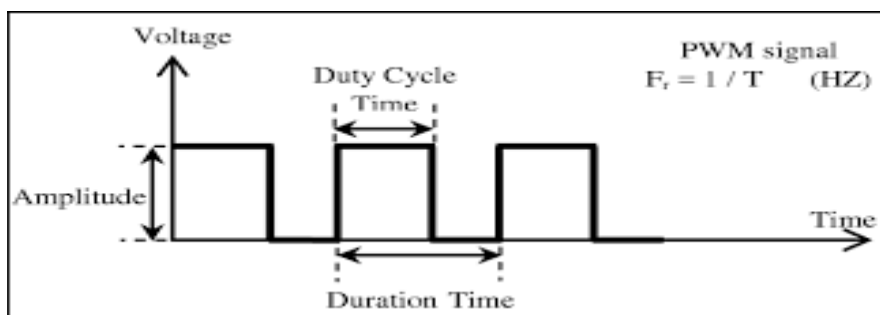


Fig 2 : Diagram of PWM signal

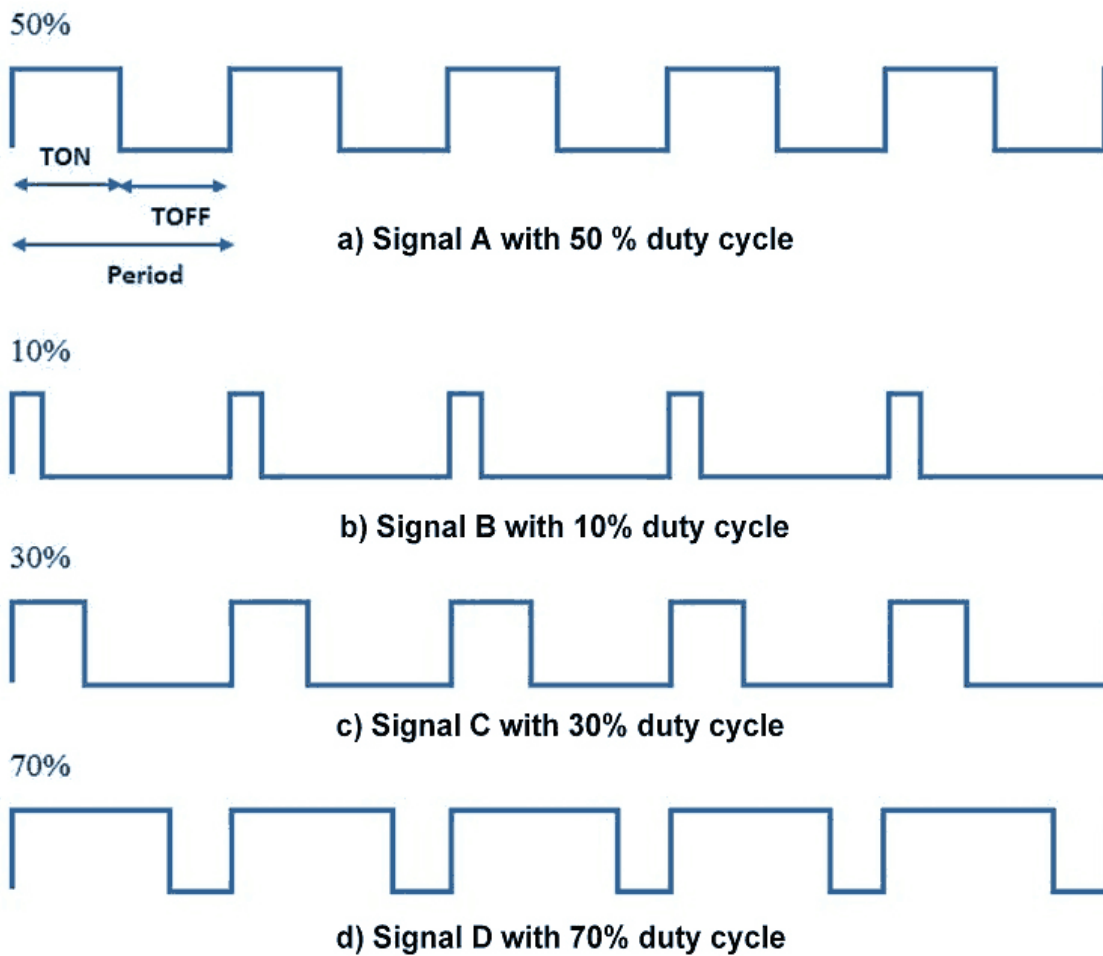


Fig 3 : Diagram of different PWM signal with different duty cycle

2) Implementation Design

Most of the implementation remain same as from previous lab now for brightness we have used an integer "counter" which will be incremented on each "rising edge of clock" . Now as counter is increasing with time so to maintain a uniform brightness of 4 LED's we have to use periodic sequence which can be obtained by using the modulo operator .

*In this case we have used "2200" to take counter modulo .
As brightness of "Leftmost 7 segment LED display " is
to be highest basically 100% , so we don't apply any condition
for its brightness. But for other remaining "3" 7 segment LED
display we have applied condition as follows :*

Position of 7 segment LED display from right side	ON condition
1 (rightmost LED)	(counter mod 2200) < 100
2	(counter mod 2200) < 500
3	(counter mod 2200) < 1200

Table 1 : condition used for brightness

Position of 7 segment LED display from right side	Duty Cycle (%) / Brightness in percentage
1 (rightmost)	$\frac{100}{2200} = 4.54 \%$
2	$\frac{500}{2200} = 22.73 \%$
3	$\frac{1200}{2200} = 54.54 \%$
4 (leftmost)	100 %

Table 2 : LED duty cycle

3) *Simulation Waveform for 4 digit 7 segment display with varying LED brightness*

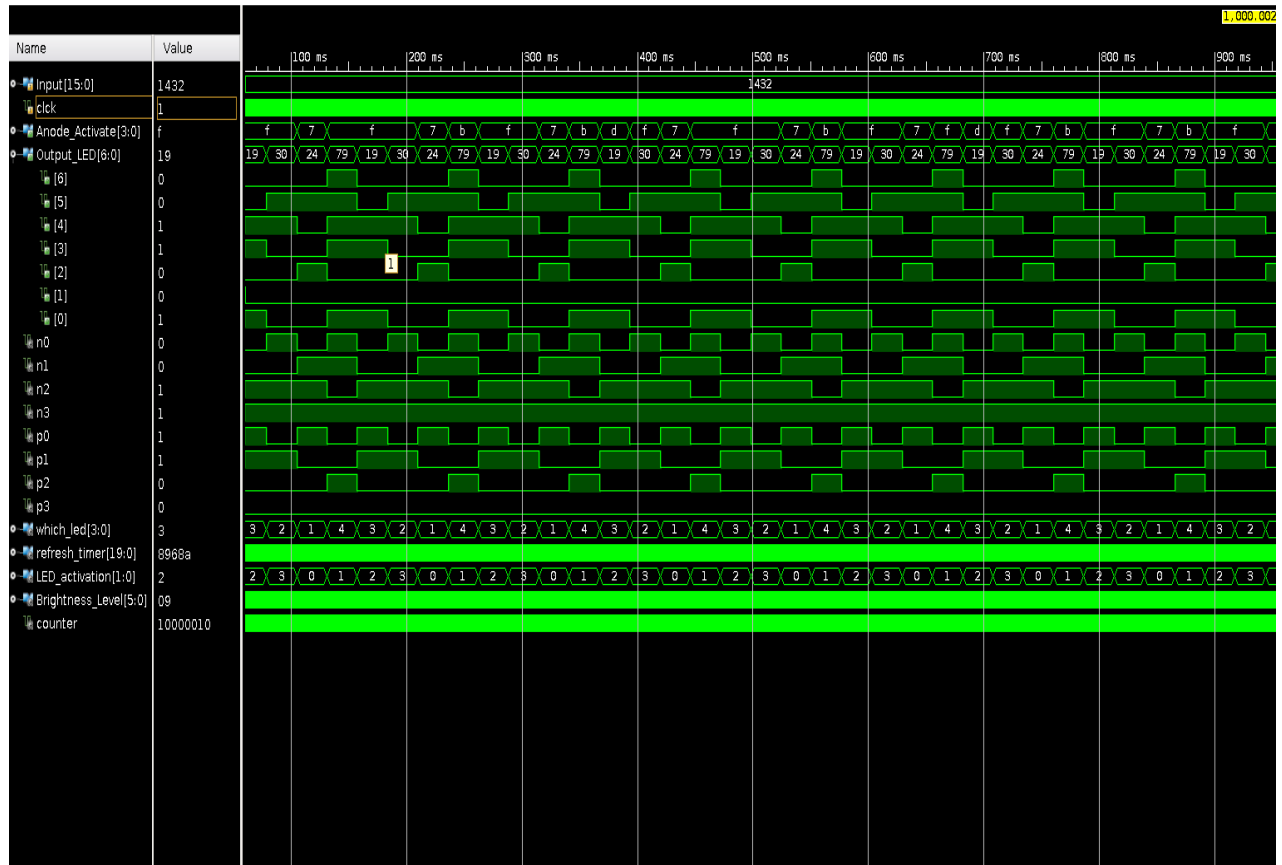


Fig 4: Waveform of 4 segment LED with different brightness

4) Digital Circuit for 4 – digit 7 Segment Display with different brightness

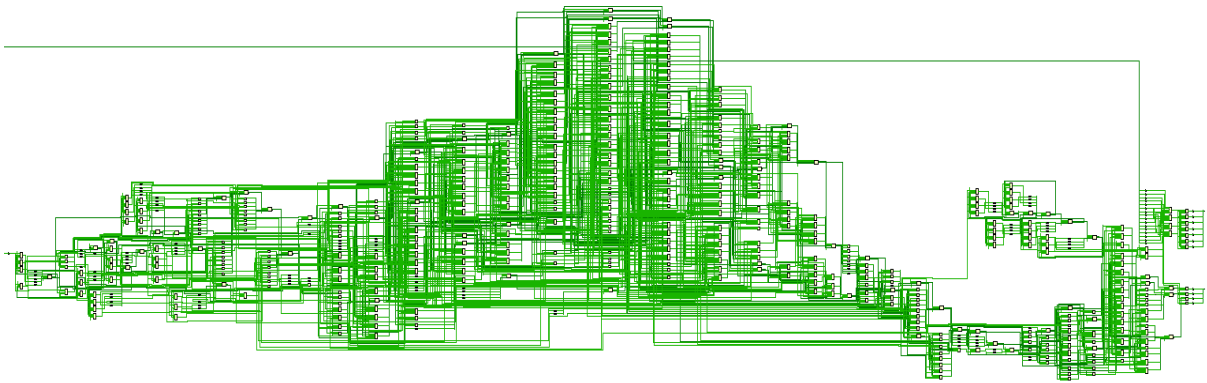


Fig 5 : Complex Digital circuit for LED brightness control

5) Resource Utilisation

- a) LUT Memory =0
- b) LUT logic = 373
- c) DSP =0
- d) Flip Flops =54
- e) BRAM = 0

6) Some other relevant diagram for resource utilisation

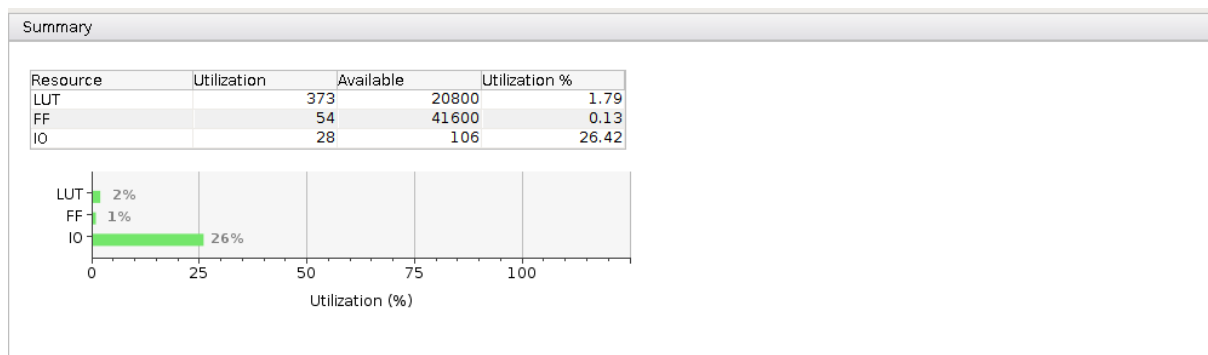


Fig 6 : Summary


Primitives		
Ref Name	Used	Functional Category
LUT6	149	LUT
LUT1	100	LUT
LUT3	83	LUT
CARRY4	66	CarryLogic
FDRE	54	Flop & Latch
LUT5	48	LUT
LUT2	42	LUT
LUT4	24	LUT
IBUF	17	IO
OBUF	11	IO
BUFG	1	Clock

Fig 7 : Primitives

Hierarchy				
Name	1	Slice LUTs (20800)	Slice Registers (41600)	Bonded IOB (106)
LED_brightness		373	54	28
				1

Fig 8 : Hierarchy

7) Some photographs of FPGA Board

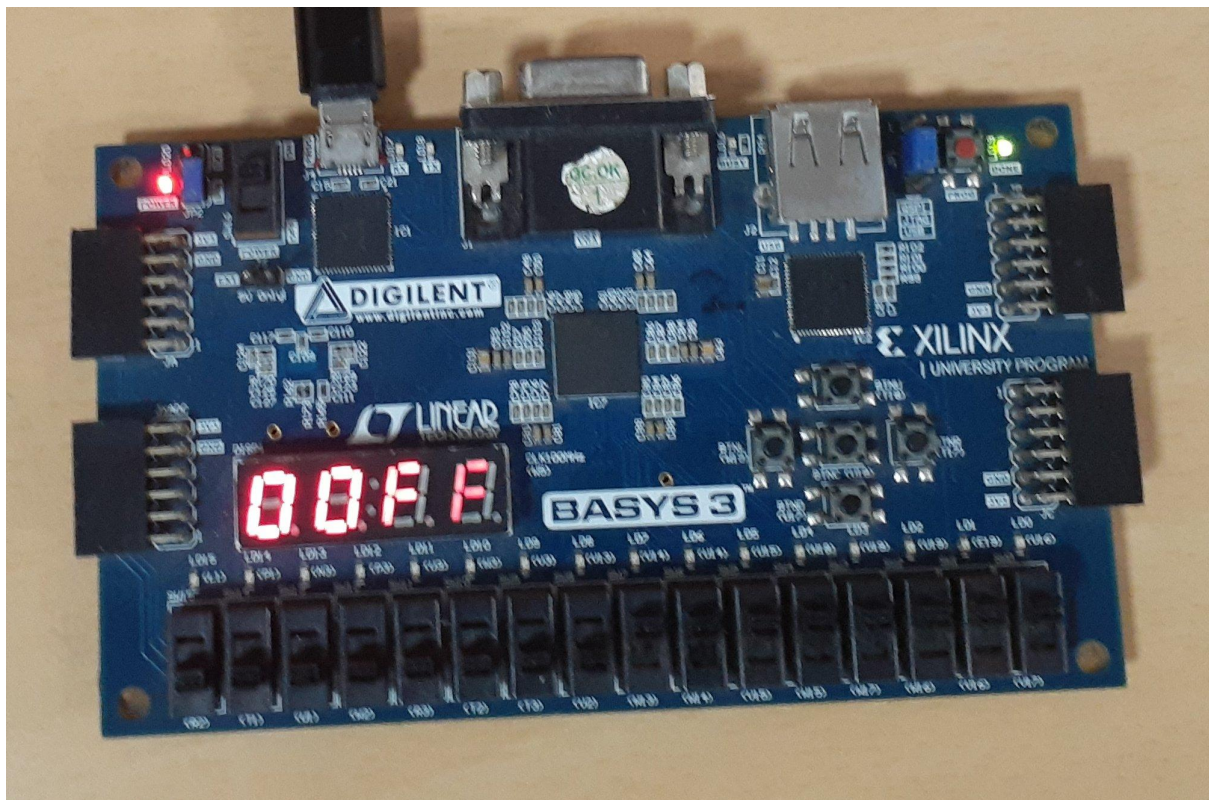

(a)